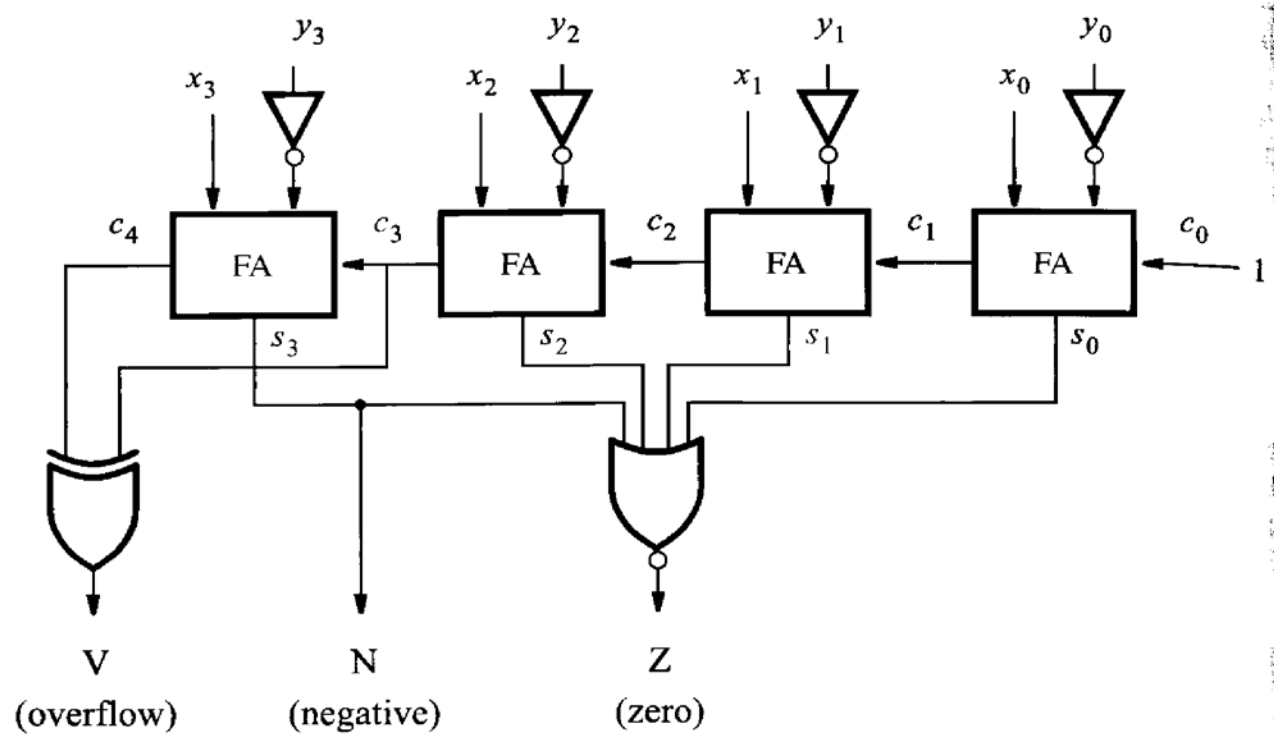



Cs 343
Spring 2017
Lab 1
Part 3

Using the procedure described in Comparator Tutorial Lab
Design:

- Using 1 bit Full-adder and gates DESIGN (write VHDL CODE) for 4 bit subtractor unit as shown in the figure below.
- In addition to the arithmetic result of the subtraction, you have to display a bit Z=1 if the result is zero, N=1 if the result is negative, and V=1 if the result is overflow.
- Create a component for this unit and include in your package.
- Verify all your designs in simulation
- Program the FPGA board and verify it works correctly.
- Using the component you have designed above and gates, multiplexers,, design 8 bit adder/ subtractor unit. Verify it in simulation and program the board.
- Write a detailed report following format given to you.



An n -bit ripple-carry adder

 

Denote by Δt time 1-Bit Full adder computes addition of two bits and carry.

Question: How much time it takes to compute the sum of two 32 bits words ?